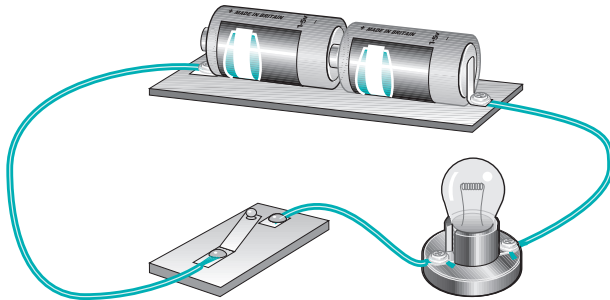



# Drawing circuits



This is a picture of a circuit ...



... and this is the **circuit diagram**.

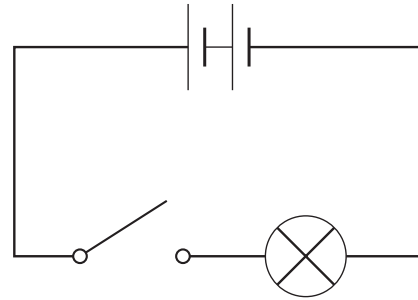

1. Draw the **symbols** for:

**a)** a bulb



**b)** a cell





**c)** an open switch





2. Draw circuit diagrams for these circuits. The first one has been started for you.

**a)**

 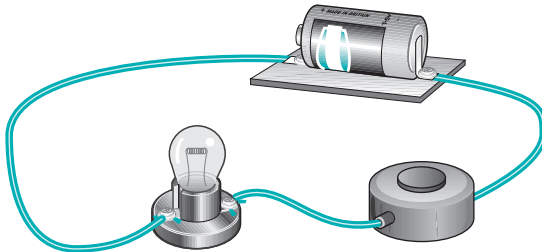

**b)**

 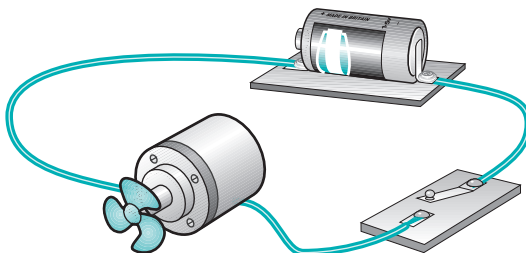

**c)**

